

ELECTRONICS TODAY

# electronics today international

JULY 1977

35p

## NERVOUS TENSION?

LEARN TO RELAX  
WITH OUR  
GSR MONITOR

8-PAGE  
**DATA**  
SUPPLEMENT

TV GAMES RIFLE  
ACTIVE FILTERS  
TACHOMETER  
MICROAMP  
MPU CALCULATOR REVIEW

NEWS . . . CONSTRUCTION . . . DEVELOPMENT . . . AUDIO

WIRING PEN OFFER

## BE A CATHODE RAY COWBOY WITH OUR

# TV GAMES RIFLE

FROM CIRCUIT AND TEXT BY WATFORD ELECTRONICS

THE TV GAMES UNIT featured in our May '77 issue has provision for the addition of two rifle games. In both games a target appears on the TV screen and the object is to 'hit' this with the TV rifle. When the trigger of the rifle is pulled a shot counter is incremented by one and if the rifle is on target the hit counter is incremented, a hit noise produced and the target blanked for a while.

The difference between the two game options is that in one the target moves randomly about the screen and in the second the target traverses the screen from left to right under the control of the manual serve button.

Unlike the other games, the score does not appear on the screen during the game since this might confuse the player, instead the score appears after 15 shots. The score is displayed with the number of shots (i.e. 15) on the left and the number of hits on the right.

### Seeing the light

The rifle uses a photodarlington to detect the target on the TV screen but relies on careful construction of the optics involved to ensure adequate sensitivity is obtained from the unit. We also arranged for the rifle to ignore any sources of light other than the target on the TV screen.

Though we called this project a TV rifle game we finally settled on what might more accurately be described as a pistol. The general method of construction used in the pistol is shown in Fig. 1.

### Getting started

The butt is made from a fairly hard wood and after being fashioned to the shape shown in

the drawing, the top was dished with a half round file to accommodate the barrel. The next step is to drill a hole vertically through the butt to take the connecting cable between the pistol and games unit. The trigger switch is mounted by drilling two holes, one above the other, and chiselling out the remaining wood to form an oblong hole. A small aluminium plate was then drilled to accept the switch and two small wood screws used to secure the plate to the butt.

### Roll out the barrel

The barrel is made from 28mm dia. metal tube 8½in. in length. To fit it to the butt two holes were drilled at one end, and two further holes drilled diametrically opposite the first pair. By passing a screwdriver through the top holes the barrel may be secured to the butt.

The lens used in the pistol had a focal length of 2½in. and came from an old jeweller's eye glass,

this was mounted in a B9A valve screening can. The photodarlington should be carefully positioned at the focal point of the lens. We mounted the photodarlington on a piece of veroboard which enabled us to slide it back and forth until its position was correct.

The assembly may then be mounted in the barrel.

### End in sight

The front sight was formed from a 4BA bolt which was filed to provide a sight tip. The rear sight is formed from a ⅜in. wide strip of aluminium about 2½in. long. One end is bent up and a 'V' slot filed with a needle file.

At this stage the p.c.b. may be assembled. The only thing to note about the components used is that they must be as small as possible, we used tantalum beads for C3, C5 and sub miniature electrolytic types.

When the board has been assembled wire it to


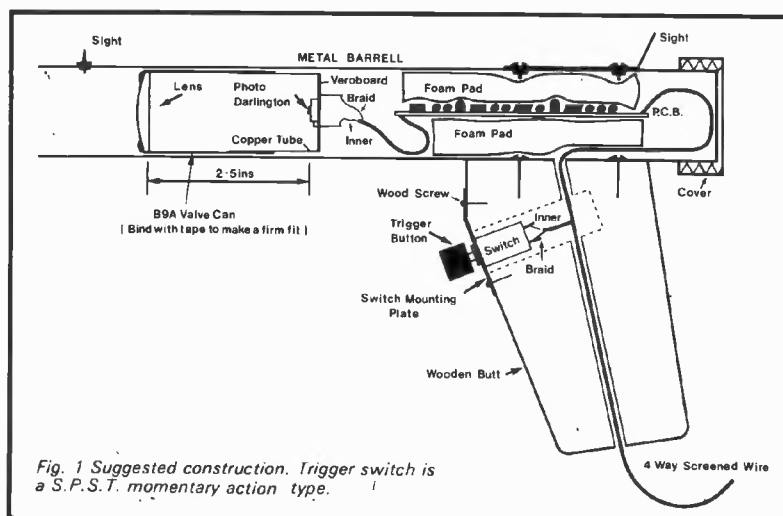


Fig. 1 Suggested construction. Trigger switch is a S.P.S.T. momentary action type.

 



## HOW IT WORKS

R1 220 k  
R2 10 k  
R3 1 M  
R4 5k6  
R5 47 k  
R6 1 M  
R7 470 k  
R8 4k7  
R9 470 k  
R10 470 k  
R11 560 R  
R12 10 k

C1	220p polystyrene
C2	1 $\mu$ 16 V electrolytic
C3	1 $\mu$ 35 V tantalum
C4	1 n polystyrene
C5	1 $\mu$ 35 V tantalum
C6	10 $\mu$ 16 V electrolytic
C7	10 $\mu$ 16 V electrolytic
C8	1 $\mu$ 16 V electrolytic



Q1 2N5777  
Q2 BC212L  
IC1 741  
IC2 555  
IC3 CD4011

PCB  
Trigger switch - see text  
Lens - 2½" focal length, 1" diameter  
Metal tube 8½" long  
Wood for butt  
4 core screened cable  
Misc. hardware for sights etc.  
A complete kit is available from Watford Electronics, including lens, tube and butt.


When the target is detected, the output of IC1 falls and triggers IC2 which is arranged to operate as a monostable. Pin 3 of IC3 will go high. Q2 is included to make IC2 re-triggerable; its out-

C6 decouples the supply rail.

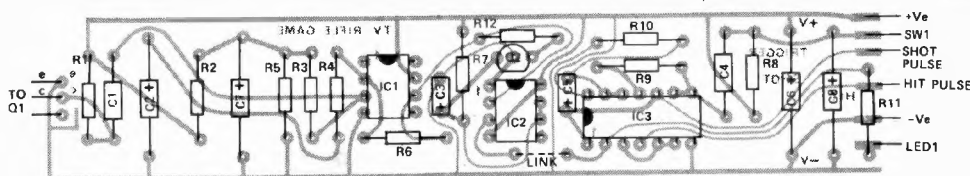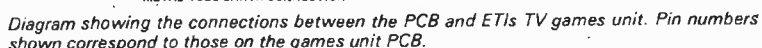**The cost of the Watford Electronics kit for this project is £10.50.**



# TV GAMES RIFLE

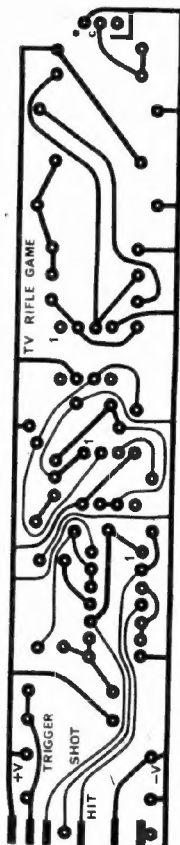

the trigger switch and to the connecting cable. It may then be mounted at the rear of the barrel by gluing it to a foam pad which may in turn be stuck to the barrel.

The connecting wire we used was four core screened cable and should be connected to the games unit as follows: (via DIN plug)

0V	to pin 5
6V	to pin 3
Hit pulse	to pin 1
Shot pulse	to pin 4

## Testing

The games unit should now be connected to your TV and the brilliance control of the TV adjusted until the target is bright and the background just visible. If the rifle is now aimed at the target, at close range initially, the 'On Target' LED should glow and a blip should be heard from the speaker when the trigger is pressed.

To adjust the sights use the score display which appears at the end of the game. Block off all the screen except one digit of the score

The sight may then be adjusted so that the hit LED is on when the pistol is aimed at the score.


## To play

Select the rifle option required with SW2 and press the reset and serve buttons. The target should appear on the screen and bounce around the screen until hit.



The PCB layout is shown full size on the left. Above is a picture showing the games rifle.
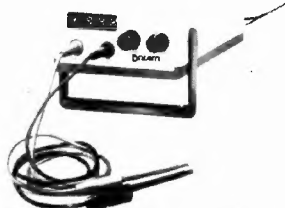
## Big saving, good looking, fast checking NEW Doram DIGITAL MULTIMETER—BUILD IT YOURSELF AND SAVE UP TO £40!



KEY DATA	
Volts DC	200mV, 2V, 20V 200V, 1000V Input impedance 4.2MΩ Maximum sensitivity 100μV
Volts AC	200mV, 2V, 20V, 200V, 500V Input impedance 4.2MΩ Maximum sensitivity 100μV
Current AC/DC	200μA, 2mA, 20mA, 200mA, 2A
Resistance	200Ω, 2KΩ, 20KΩ, 200KΩ, 2MΩ

A clear, functional multimeter, featuring extremely accurate digital display, in superbly styled shatterproof carry-case. It could cost £100! But the complete Doram kit with case, printed circuit board, leads and all components is yours for just £54.50 plus £4.36 VAT.

Based on Ferranti technology with accuracy  $\pm 0.6\%$ , the new Doram Multimeter is an indispensable tool at a terrific saving. Measurement is indicated by a 3½ digit display updated twice per second—display flashes to indicate overload.

And it saves you money before it's even built!

## DEPEND ON DORAM

Thousands of kit makers do for top value and modern technology.  
Doram Electronics Ltd, PO Box TR8, Wellington Road Industrial Estate, Wellington Bridge, Leeds, West Yorkshire LS12 2JF.  
Registered in London No. 1156856. Directors: R. A. Marler, D. J. Turner, F. Chable.

## Yes, I want to save up to £40

Please send me (subject to availability) ... complete kit(s) for Doram DIGITAL MULTIMETER at (£54.50 + £4.36 VAT incl. p & p) total £58.86. I understand I can return the unused kit(s) within 7 days and claim my money back if kit(s) returned undamaged in the form received and ready for re-sale.

Please send me ..... complete DORAM KITS CATALOGUE(s) showing an additional 25 kits, at 25p each.

I enclose cheque/PO value

NAME (BLOCK CAPITALS)

ADDRESS

TOWN

COUNTY

POST TO DORAM ELECTRONICS LTD., DEPT. EM2, PO BOX TR8, LEEDS WEST YORKSHIRE LS12 2JF



## Wilmslow Audio

### THE firm for speakers!

Send 10p stamp for the world's best catalogue of Speakers, Drive Units, Kits, Crossovers, etc., and discount price list

ACT ● AUDAX ● BAKER ● BOWERS & WILKINS  
● CASTLE ● CELESTION ● CHARTWELL ●  
COLES ● DALESFORD ● DECCA ● EMI ● EAGLE  
● ELAC ● FANE ● GAUSS ● GOODMAN'S  
HELME ● I.M.F. ● ISOPHON ● JR ● JORDAN  
WATTS ● KEF ● LEAK ● LOWTHER ●  
McKENZIE ● MONITOR AUDIO ● PEERLESS ●  
RADFORD ● RAM ● RICHARD ALLAN ● SEAS ●  
TANNOY ● VIDEOTONE ● WHARFEDALE

## WILMSLOW AUDIO Dept. ETI

SWAN WORKS, BANK SQUARE, WILMSLOW,  
CHESHIRE, SK9 1HF

Discount HiFi, etc., at 5 Swan Street and 10 Swan  
Street

TEL: WILMSLOW 29599 FOR SPEAKERS  
WILMSLOW 26213 FOR HIFI